

BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI  
(MID SEMESTER EXAMINATION MO/2023)

CLASS: B.TECH/IMSC.  
BRANCH: BT/CIVIL/CHEMICAL/MECH/PIE/FT/PHYSICS

SEMESTER : I  
SESSION : MO/2023

SUBJECT: EE101 BASIC OF ELECTRICAL ENGINEERING

TIME: 02 Hours


FULL MARKS: 25

**INSTRUCTIONS:**


1. The question paper contains 5 questions each of 5 marks and total 25 marks.
2. Attempt all questions.
3. The missing data, if any, may be assumed suitably.
4. Tables/Data handbook/Graph paper etc., if applicable, will be supplied to the candidates

Q.1(a) Define (i) bilateral and unilateral elements (ii) active and passive elements. [2] CO BL

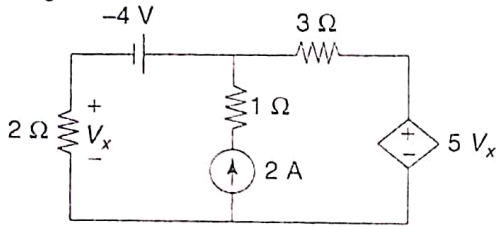
Q.1(b) Apply mesh analysis to calculate the current through the  $3\Omega$  resistor and the voltage  $V_x$  of the given circuit. [3] CO1 BL1  
[3] CO1 BL3



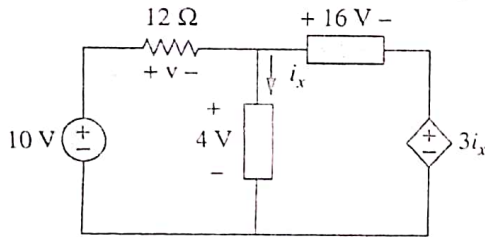
Q.2(a) Apply KVL/KCL to calculate the value of  $i_x$  and  $v$  in the given circuit. [2] CO1 BL3



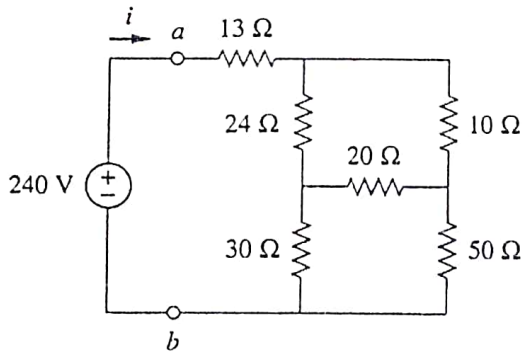Q.2(b) Apply star delta conversion, to estimate the equivalent resistance  $R_{ab}$  across the terminals a-b and the current  $i$  in the circuit below. [3] CO1 BL3



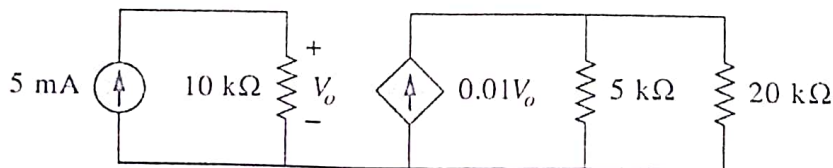
Q.3(a) For the circuit given below, calculate the current, voltage and power associated with the  $20k\Omega$  resistor. [2] CO1 BL3



Q.3(b) Two impedances of  $(14 + j5)\Omega$  and  $(18 + j10)\Omega$  are connected in parallel across a 200 V, 50 Hz AC supply. Determine (i) the current in each branch and total current, (ii) the power factor of each branch, and (iii) draw the phasor diagram. [3] CO2 BL3

include briefly about operators of the following applied to the

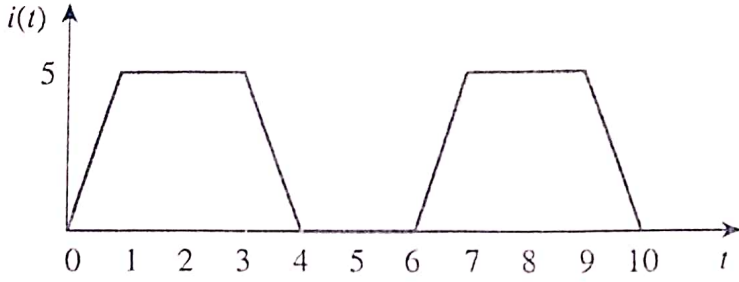- Q.4(a) Define the RMS value and average value of a signal. [2] CO2 BL1
- Q.4(b) Calculate the RMS and average value of the waveform shown below: [3] CO2 BL3



- Q.5(a) Define (i) Q-factor and (ii) Bandwidth [2] CO2 BL1
- Q.5(b) A series resonant circuit has an impedance of  $500 \Omega$  at resonant frequency. Cut-off frequencies are 10 kHz and 100 Hz. Calculate (i) resonant frequency, (ii) value of L, C, and (iii) quality factor at resonant frequency. [3] CO2 BL3

:::::18/10/2023:::::